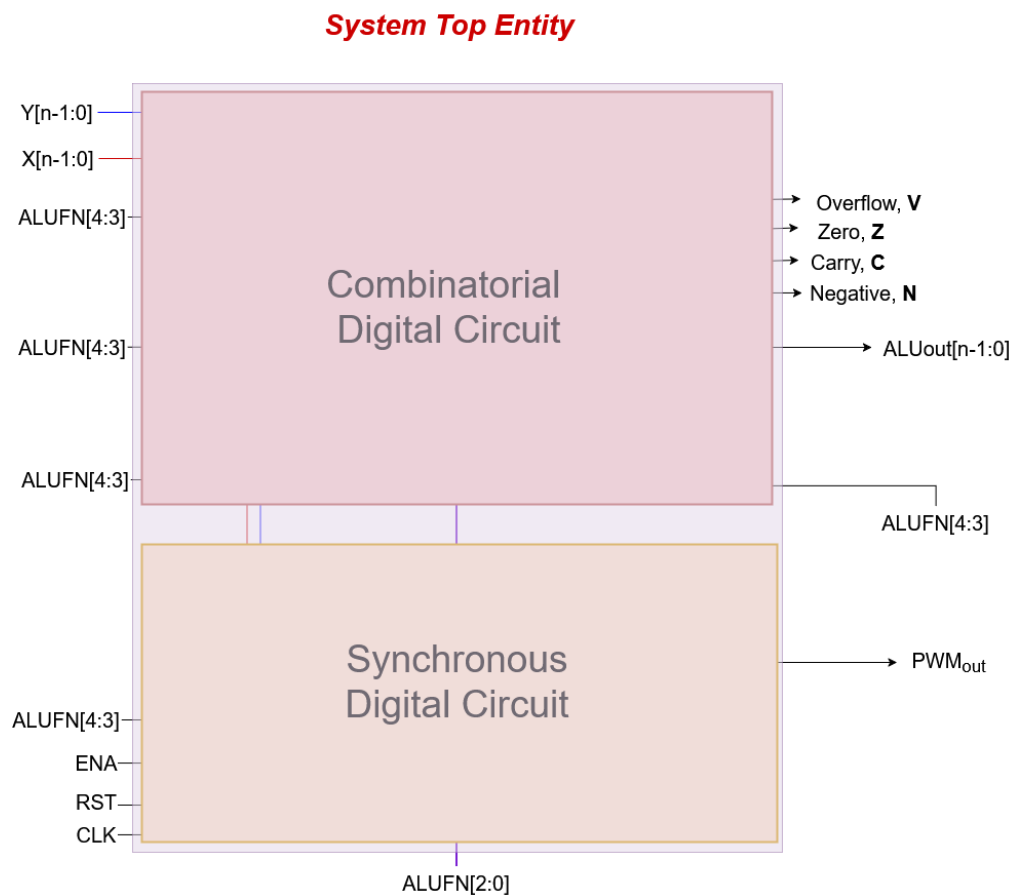


[Figure 2a: I/O interface of the DE10-Standard FPGA board](#)


[Figure 2b: I/O interface of the DE2-115 FPGA board](#)

**Figure 2 : I/O interface of the DE10-Standard and the DE2-115 FPGA boards**


The digital system is composed of two concurrent parts, combinatorial and synchronous, as shown in Figures 3 and 4.



**Figure 3: Digital System subparts**

 

**Figure 4: Digital System subparts architecture**

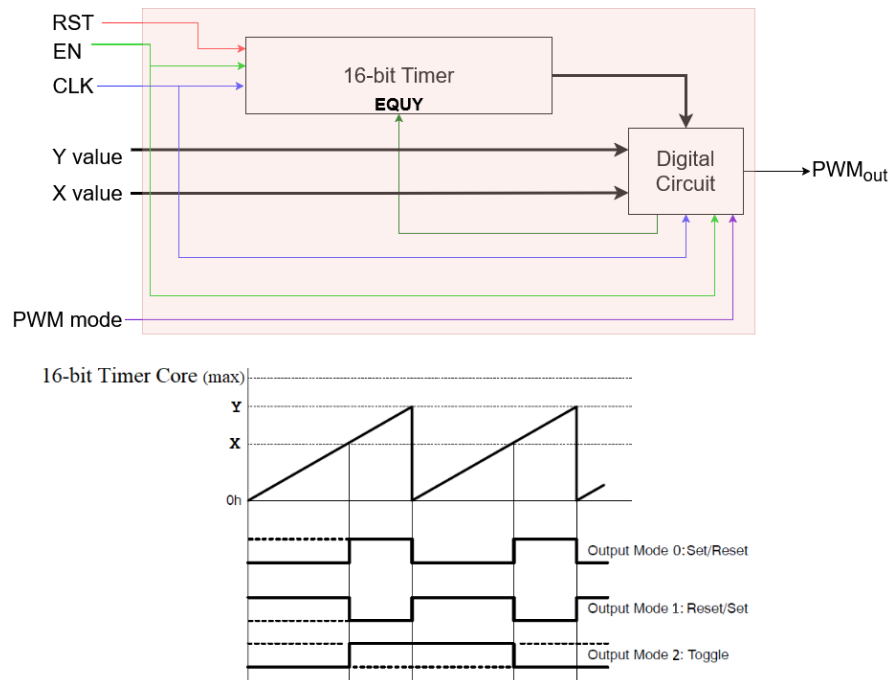

**Figure 5: PWM output unit architecture**

The whole system must be connected to the Altera board interfaces according to the following diagram:

 
 


Figure 6: Digital system with I/O interface

The ISA of the combinatorial subpart is given in Figure 7, which is associated with the LAB1 task.

Function Type	Decimal value	ALUFN	Operation	Note
<b>PWM Output</b> ( <i>Y and X are 16-bit width</i> )	0	00000	PWM MODE0	PWM Mode is Set/Reset
	1	00001	PWM MODE1	PWM Mode is Reset/Set
	2	00010	PWM MODE2	PWM Mode is Toggle
<b>Arithmetic</b> ( <i>Y and X are 8-bit width</i> )	8	01000	Res=Y+X	
	9	01001	Res=Y-X	Used also for comparison operation
	10	01010	Res=neg(X)	
	11	01011	Res=Y+1	Increment of Y in one
	12	01100	Res=Y-1	Decrement of Y in one
	13	01101	Res=swap(Y)	Res=(YLSHW, YMSHW)
<b>Shift</b> ( <i>Y and X are 8-bit width</i> )	16	10000	Res=SHL Y,X(k-1 to 0)	Shift Left Y of $q \triangleq X(k-1 \dots 0)$ times Res=Y(n-1-q...0)#(q@0) <b>When <math>k = \log_2 n</math></b>
	17	10001	Res=SHR Y,X(k-1 to 0)	Shift Right Y of $q \triangleq X(k-1 \dots 0)$ times Res=(q@0)#Y(n-1...q) <b>When <math>k = \log_2 n</math></b>
<b>Boolean</b> ( <i>Y and X are 8-bit width</i> )	24	11000	Res=not(Y)	
	25	11001	Res=Y or X	
	26	11010	Res=Y and X	
	27	11011	Res=Y xor X	
	28	11100	Res=Y nor X	
	29	11101	Res=Y nand X	
	30	11110	Res=Y xnor X	

Figure 7: ISA of the combinatorial subpart of digital design